

# Basic Electrical Engineering (TEE 101)

## *Lecture 13: Numerical on Theorems*

# Content

**This lecture covers  
Numerical on :**

**Superposition Theorem**




**Thevenin's Theorem**

**Norton's Theorem**
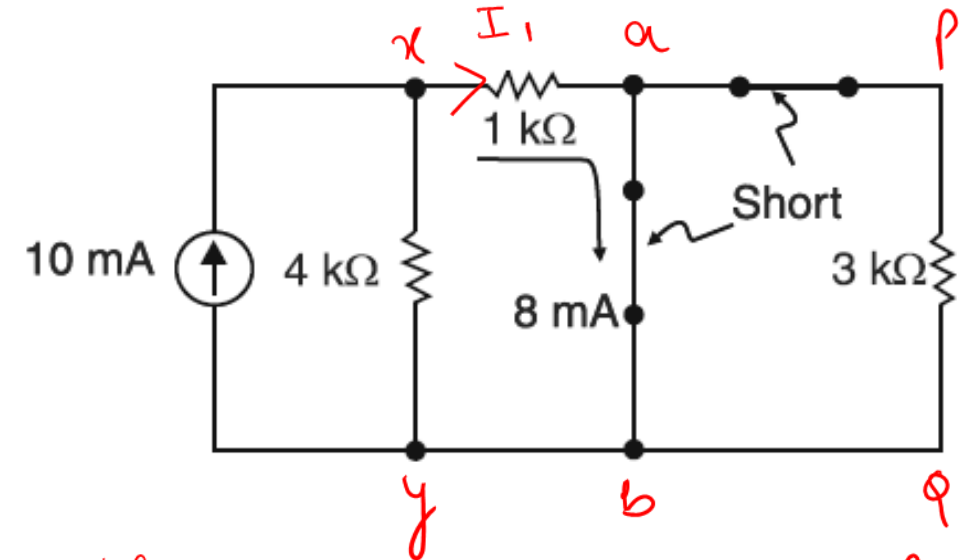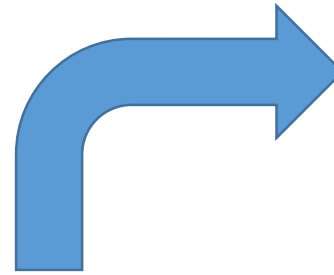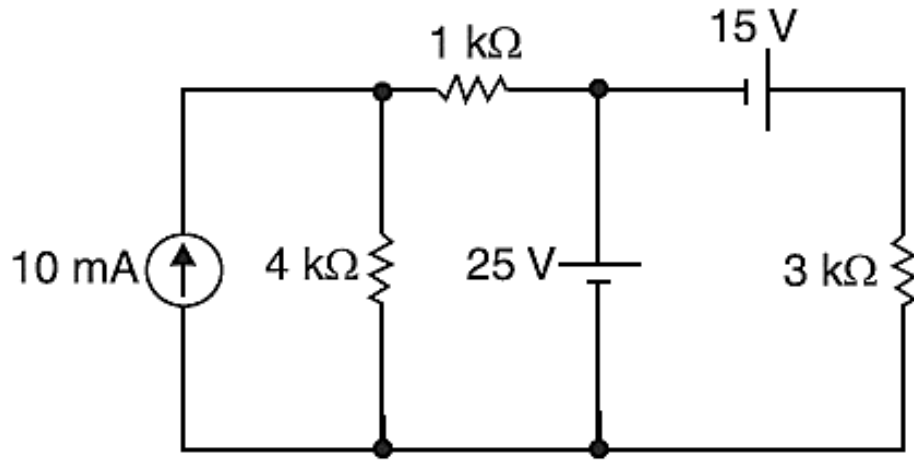
# Basic Electrical Engineering (TEE 101)

***Lecture 13(a): Numerical  
on Superposition theorem***

Using the superposition theorem, find the current through  $1\text{ k}\Omega$  resistor in Figure shown below. Assume the sources to be ideal.



**Step 1:** The current through  $1\text{ k}\Omega$  resistor due to **current source**

The current through  $1\text{ k}\Omega$  resistor due to **current source acting alone** is found by replacing  $25\text{-V}$  and  $15\text{-V}$  sources by short circuit

Let the current through  $1\text{ k}\Omega$  resistor due to **current source acting alone** is  $I_1$

Apply current division rule at  $J^n$   $x$  we get

$$I_1 = \frac{10\text{ mA} \times 4\text{ k}\Omega}{4\text{ k}\Omega + 1\text{ k}\Omega} = 8 \times 10^{-3}\text{ A}$$

$$I_1 = 8\text{ mA} \quad [\text{from } x \rightarrow a]$$

**Step 2:** The current through  $1\text{k}\Omega$  resistor due to **25 V source**

The current through  $1\text{k}\Omega$  resistor due to **25 V source acting alone** is found by replacing the  $10\text{ mA}$  current source by an open circuit and  $15\text{ V}$  source by a short circuit


Let the current through  $1\text{k}\Omega$  resistor due to  $25\text{V}$  **voltage source acting alone** is  $I_2$

Let the net current by  $25\text{ V}$  source is  $I_2'$ .

apply current division rule at  $J^{\text{th}}$  'a'

$$I_2 = \frac{I_2' \times 3\text{k}\Omega}{4\text{k}\Omega + 1\text{k}\Omega + 3\text{k}\Omega} = \frac{3I_2'}{8}$$

now, we have to calculate  $I_2'$

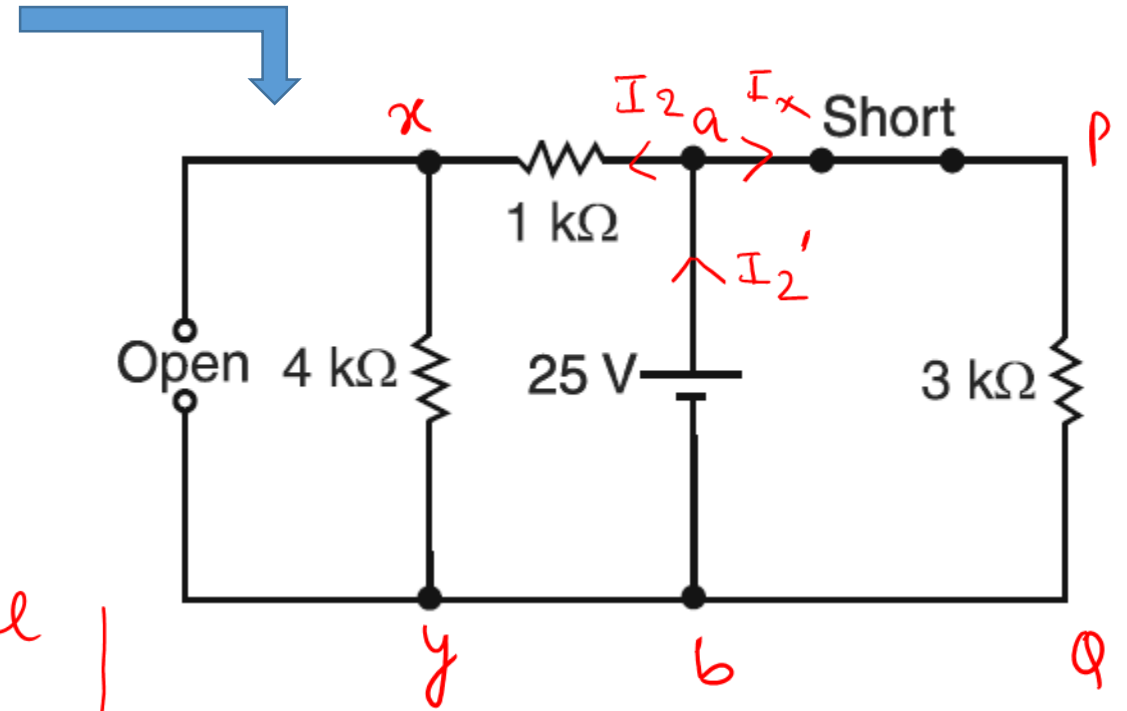

$$I_2' = \frac{25\text{V}}{R_{eq}}$$

hence  $I_2'$  is

$$I_2' = \frac{25}{15} \times 8 \times 10^{-3}\text{ A}$$

$$I_2' = \frac{40}{3}\text{ mA}$$

So, the value of  $I_2$  is  $5\text{ mA}$  (from  $a \rightarrow x$ )

$$R_{eq} = (4\text{k}\Omega + 1\text{k}\Omega) \parallel 3\text{k}\Omega$$


$$R_{eq} = 5\text{k}\Omega \parallel 3\text{k}\Omega$$

$$R_{eq} = \frac{15}{8}\text{ k}\Omega$$

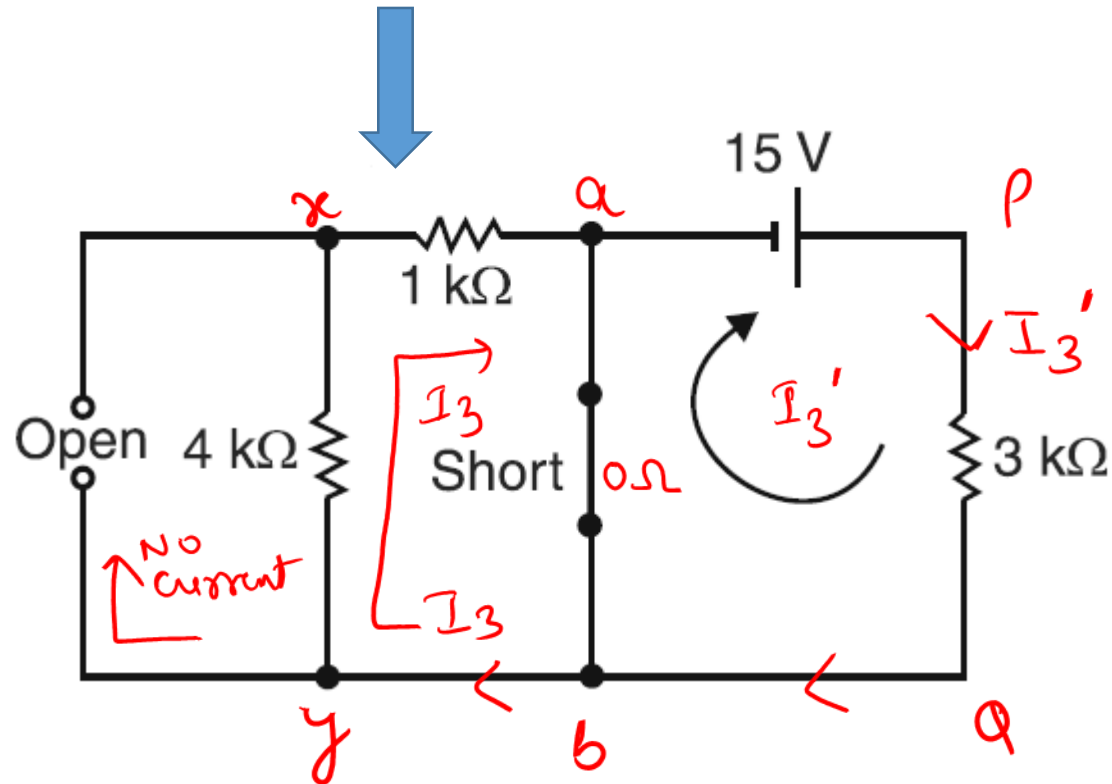**Step 3:** The current through  $1\text{k}\Omega$  resistor due to **15 V source**

The current through  $1\text{k}\Omega$  resistor due to **15 V source acting alone** is found by replacing the  $10\text{ mA}$  current source by an open circuit and  $25\text{ V}$  source by a short circuit

Let the current through  $1\text{k}\Omega$  resistor due to  $15\text{V}$  **voltage source acting alone** is  $I_3$



In this case the current ( $I_3$ ) through  $1\text{k}\Omega$  resistor can be calculated as:

apply C.D.R at  $J^a b$  we get

$$I_3 = \frac{I_3' \times 0}{4\text{k}\Omega + 1\text{k}\Omega + 0} = 0$$


i.e.  $I_3 = 0$ , hence the current will not flow through  $1\text{k}\Omega$  resistor. So, as per the Superposition theorem the net current through  $1\text{k}\Omega$  R is

$$= 8\text{mA} - 5\text{mA} + 0$$
$$= 3\text{mA} \quad \underline{\text{Answer}}$$
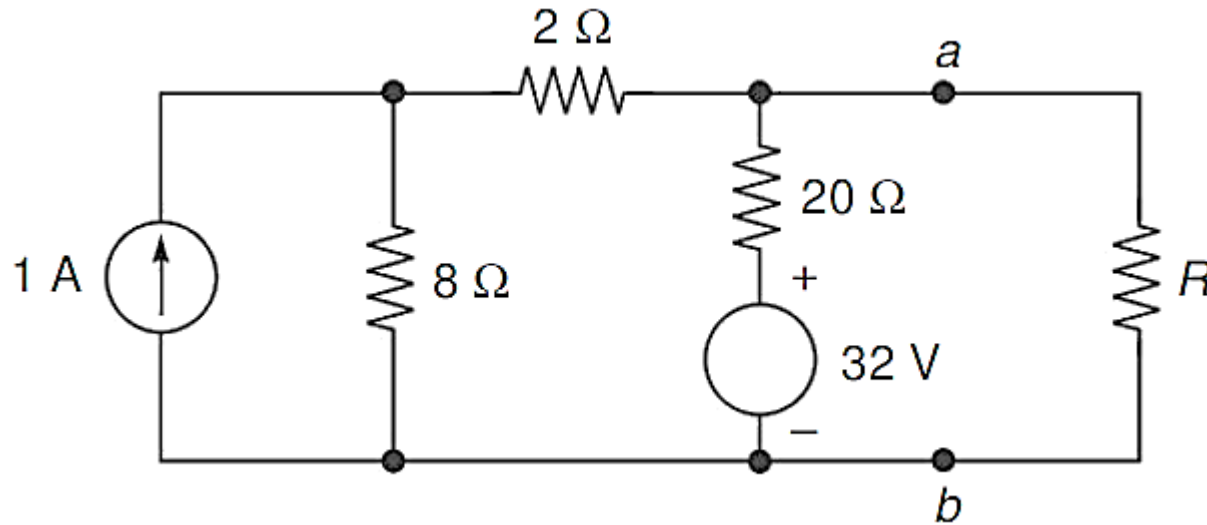
# Basic Electrical Engineering (TEE 101)


***Lecture 13(b): Numerical  
on Thevenin's Theorem***

Find the Thevenin's equivalents of the circuit of Figure shown below, as seen at terminal ab, and hence calculate the load current ( $I_L$ ) (**Assume  $R = 10 \Omega$** )



### (1) Calculate the Thevenin's Resistance ( $R_{TH}$ )

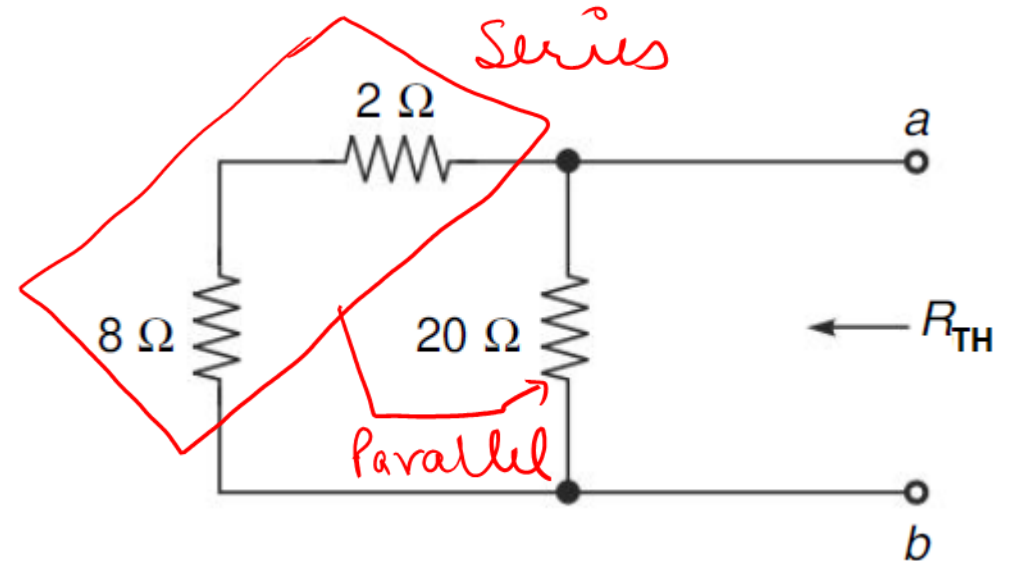(a) Thevenin's Resistance ( $R_{TH}$ ) can be calculated by replacing the 1A current source with open path and 32V source with short path.



(b)  $R_{TH}$  is calculated by removing the load and making the load terminals open!

$$R_{TH} = (8\Omega + 2\Omega) \parallel 20\Omega$$

$$= 10\Omega \parallel 20\Omega = \frac{200\Omega}{30}$$

$$R_{TH} = \frac{20}{3}\Omega$$



## (2) Calculate the Thevenin's Voltage ( $V_{TH}$ )

Remove load resistance  $R$  causing open-circuit at  $ab$ .

Replace 1A source and  $8\Omega$  resistance in parallel with it by its equivalent voltage source.

$$V_{oc} = V_a - V_b, \text{ or}$$

$$V_{oc} = V_x - V_y$$



$$V_x - V_y = 32 - 20I \quad \text{--- (1)}$$

$$I = \frac{32 - 8}{8 + 2 + 20} = \frac{24}{30} = 0.8 \text{ A}$$


$$V_x - V_y = 32 - 20 \times (0.8) = 32 - 16$$

$$V_x - V_y = 16 \text{ V or}$$


$$V_{oc} = 16 \text{ V}$$

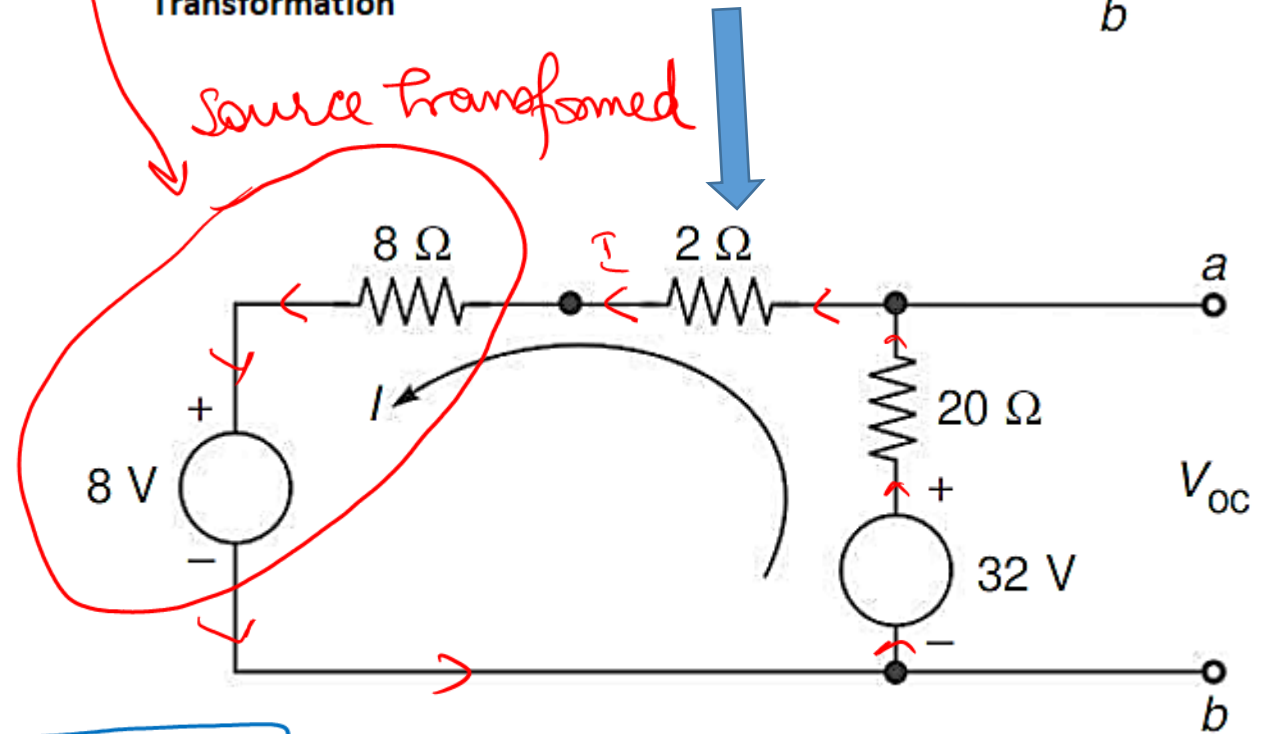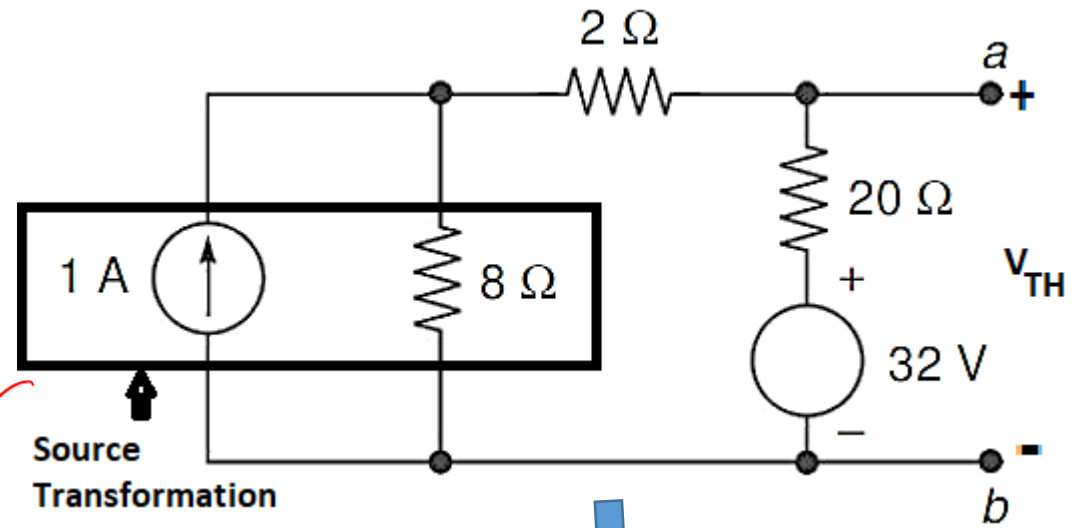

### (3) Draw the Thevenin's Equivalent

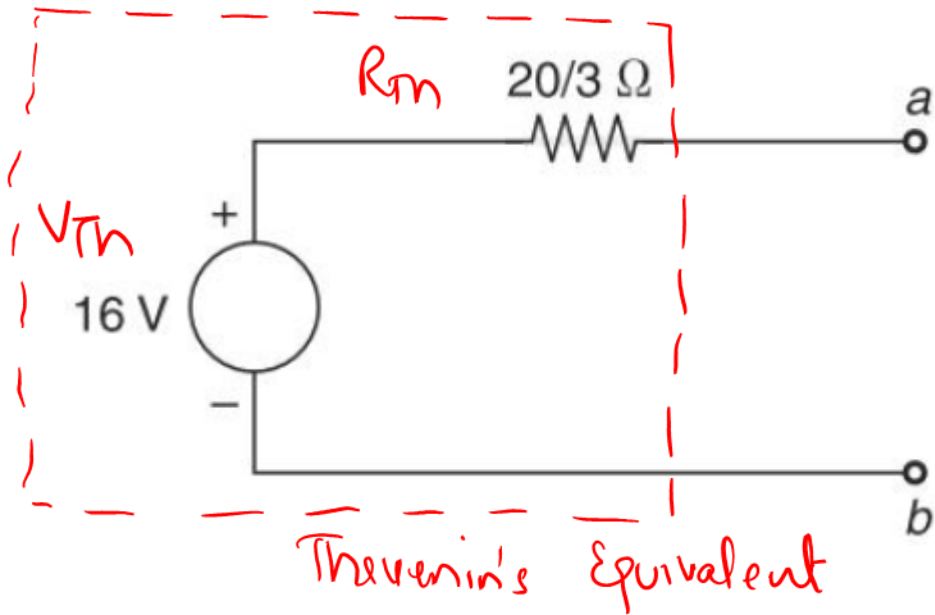
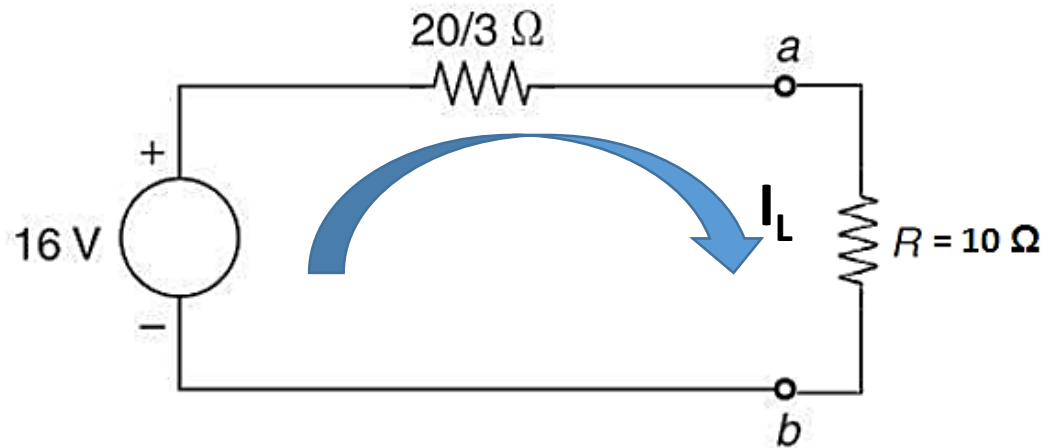
### (4) Calculate the load current ( $I_L$ )



Load current,  $I_L$  is calculated as  $\rightarrow$

$$I_L = \frac{V_{Th} \text{ (or } V_{oc})}{R_{Th} + R_L}$$

$$= \frac{16}{\frac{20}{3} + 10} = \frac{16 \times 3}{20 + 30}$$


$$I_L = \frac{48}{50} \text{ A}$$

Answer

# Basic Electrical Engineering (TEE 101)
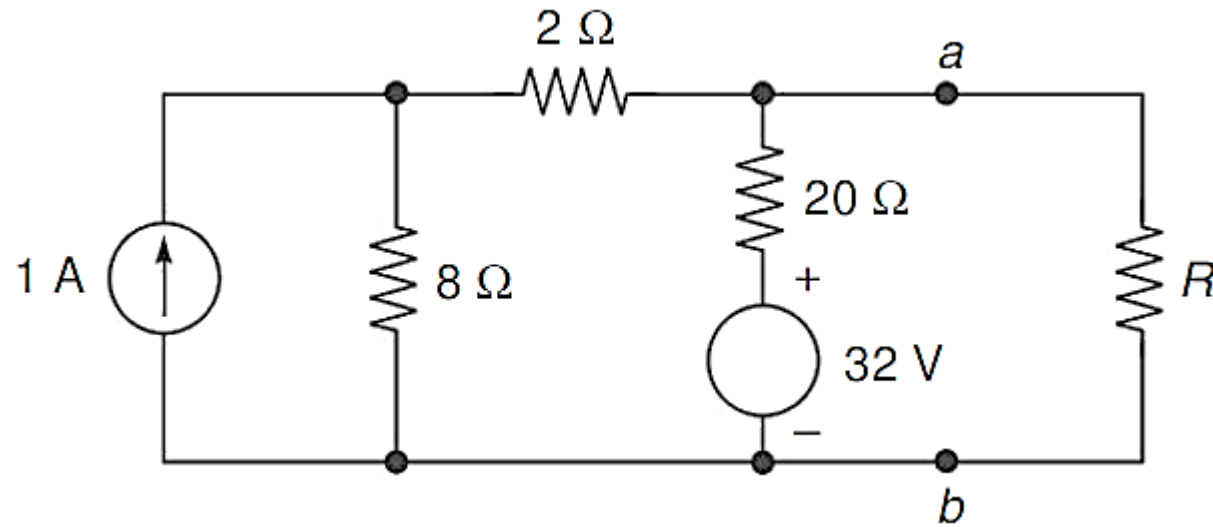
## *Lecture 13(c): Numerical on Norton's Theorem*

Find the Norton's equivalents of the circuit of Figure shown below, as seen at terminal ab, and hence calculate the load current ( $I_L$ ) (**Assume  $R = 10 \text{ ohm}$** )




To obtain the Norton's equivalent of the given network we need:  
 $\Rightarrow$  Norton's Resistance ( $R_N$ ), and  
 $\Rightarrow$  Norton's Current ( $I_N$ )
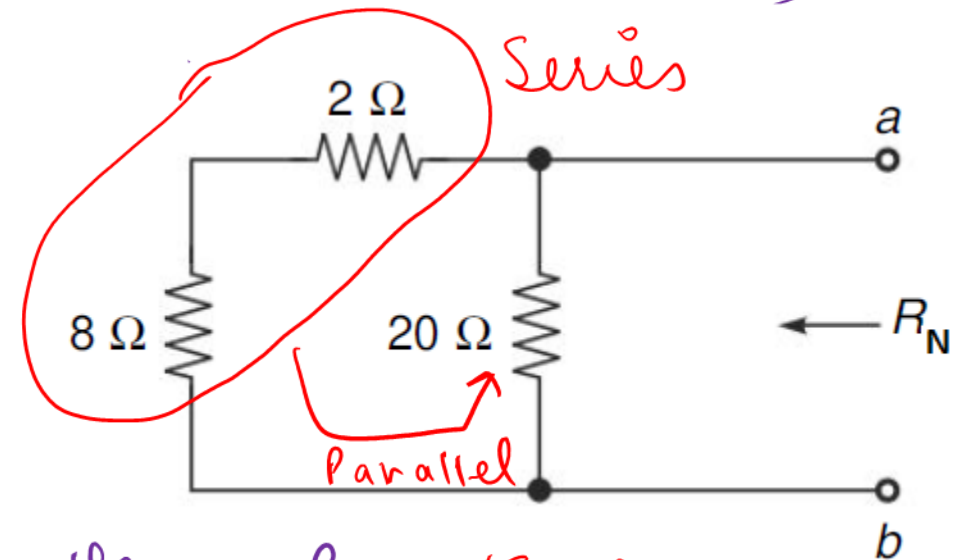
### (1) Calculate the Norton's Resistance ( $R_N$ )

Norton's Resistance ( $R_N$ ) can be calculated by replacing the 1A current source with open path and 32V source with short path.

$R_N$  is calculated in the similar manner as  $R_m$  is calculated.




hence,  $R_N = (8 + 2) \parallel 20$

$$R_N = 10 \parallel 20 = \frac{200}{30} = \frac{20}{3} \Omega$$
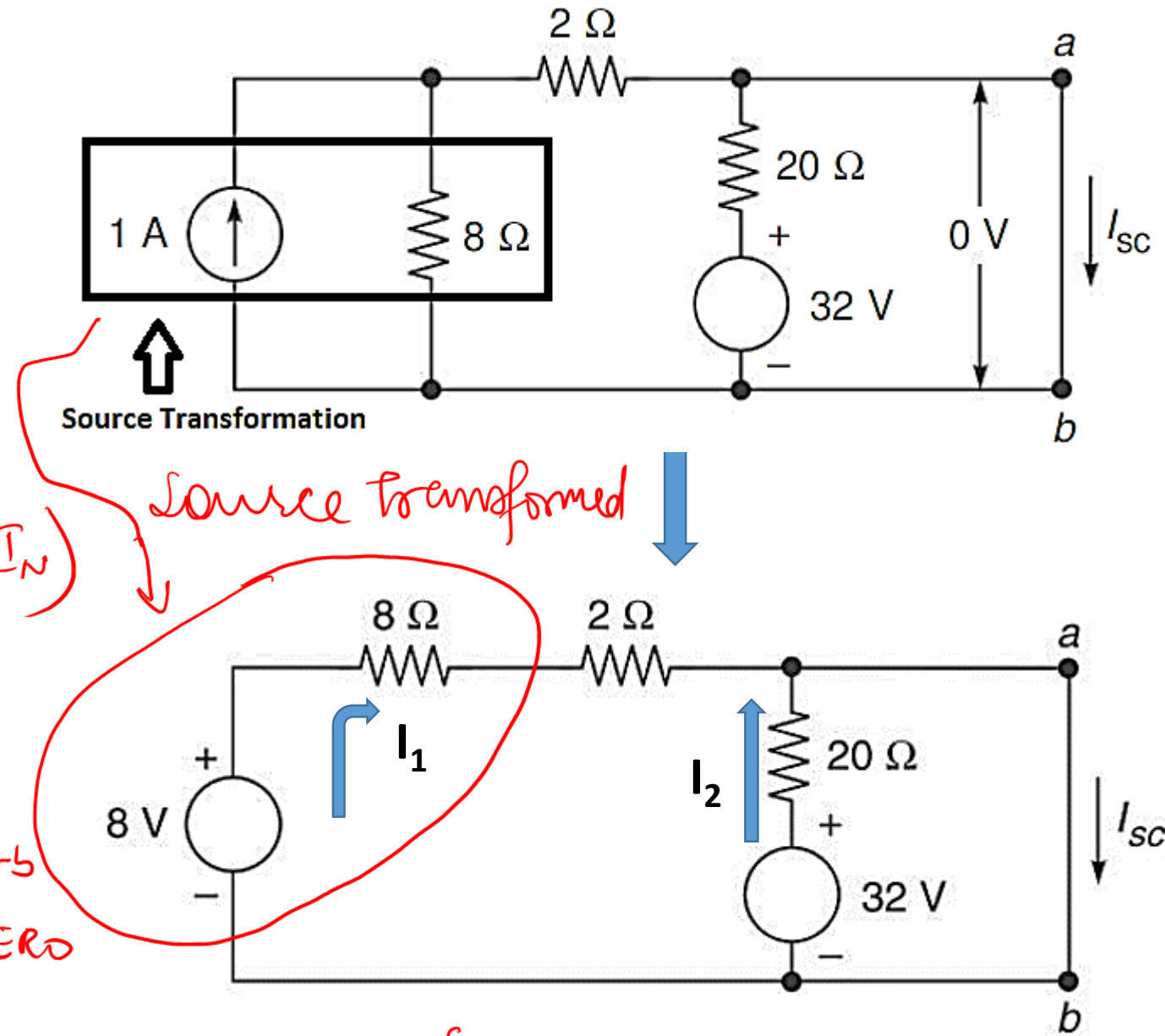
## (2) Calculate the Norton's Current ( $I_N$ )

Remove load resistance  $R$  causing open-circuit at  $ab$ .

Replace 1A source and 8X resistance in parallel with it by its equivalent voltage source.



$I_{sc} \Rightarrow$  short circuit current  
(also known as Norton's current  $I_N$ )

$I_1$  is current due to 8V source


$I_2$  " " " " 32V "

Both currents will flow in path  $a-b$   
as  $I_{sc}$  because this branch has zero  
Resistance. Hence


$$I_{sc} = I_1 + I_2 ; \quad I_1 = \frac{8}{10} = 0.8 \text{ A} ; \quad I_2 = \frac{32}{20} = 1.6 \text{ A}$$

$$\text{So } I_{sc} = 0.8 + 1.6 \\ I_{sc} = 2.4 \text{ A}$$

### (3) Draw the Norton's Equivalent

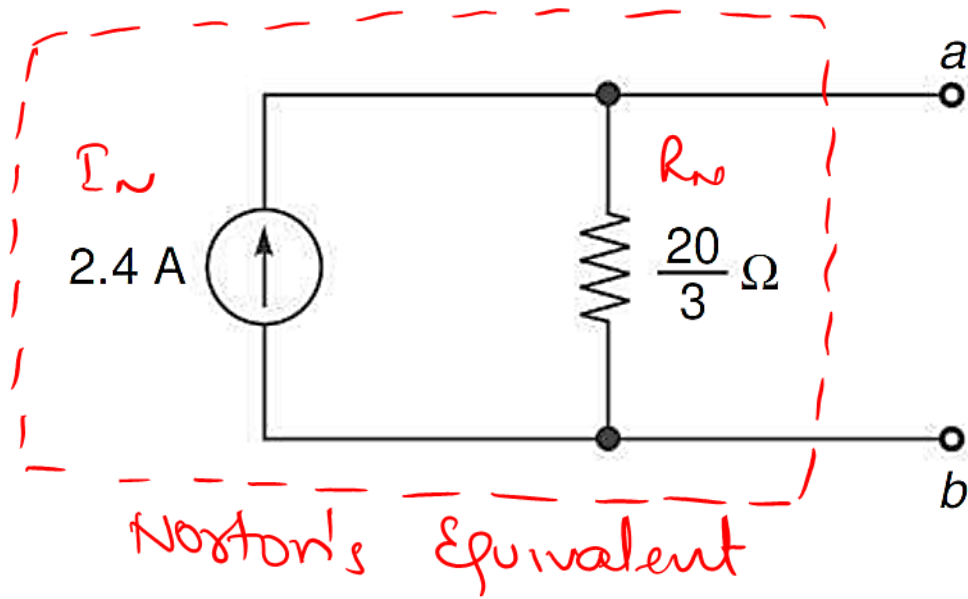
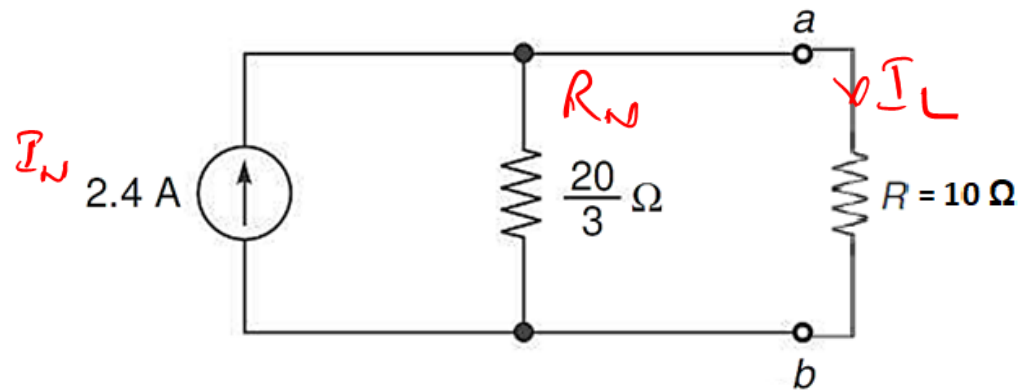
### (4) Calculate the load current ( $I_L$ )



load current,  $I_L$  is

$$I_L = \frac{I_N \times R_N}{R_N + R_L}$$

$$I_L = \frac{2.4 \times \frac{20}{3}}{\frac{20}{3} + 10} = \frac{(48/3)}{(50/3)}$$

$$I_L = \frac{48}{50}\text{ A}$$

Answer.

**Thank You**