
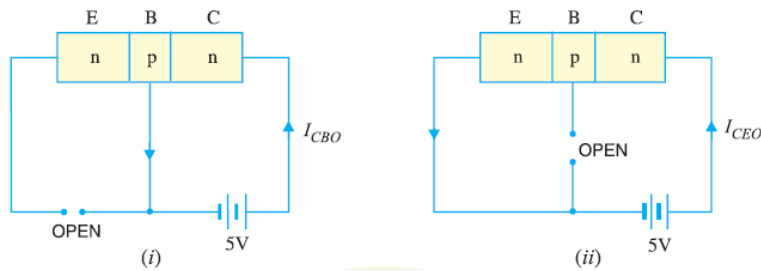


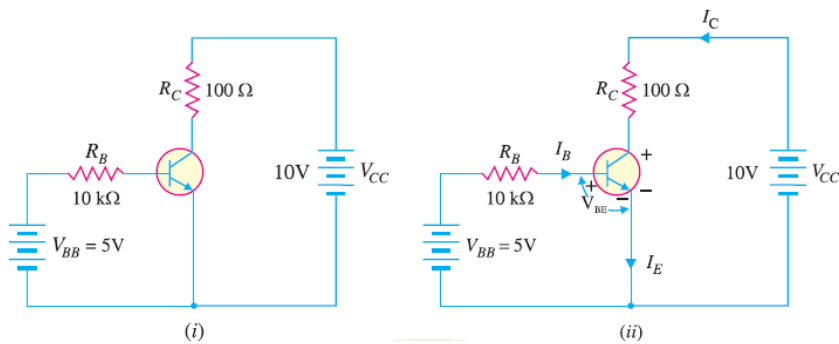
1. An n-p-n transistor at room temperature has its emitter disconnected. A voltage of 5 V is applied between collector and base. With collector positive, a current of $0.2 \mu\text{A}$ flows. When the base is disconnected and the same voltage is applied between collector and emitter, the current is found to be $20 \mu\text{A}$. Find α , I_E and I_B when collector current is 1 mA.




2. Determine VCB in the transistor circuit shown in Fig. (i). The transistor is of silicon and has $\beta = 150$.



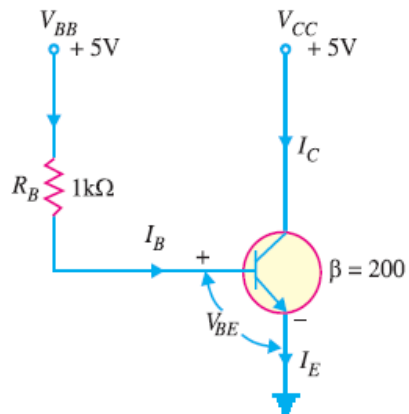3. For the circuit shown in Fig. 30, find the transistor power dissipation. Assume that $\beta = 200$.



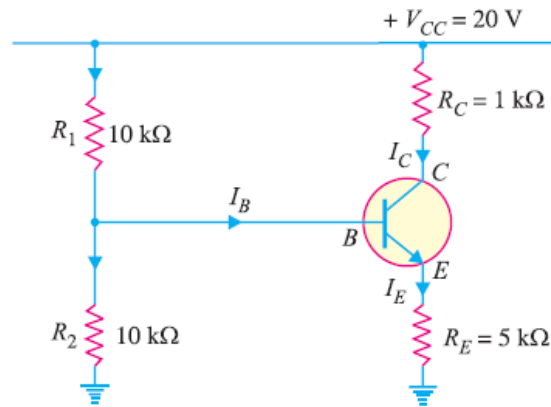4. Calculate the emitter current in the voltage divider circuit shown in Fig. find the value of I_E , V_{CE} and collector potential V_C .



5. An npn transistor circuit as shown in Fig. has $\alpha = 0.985$ and $V_{BE} = 0.3\text{ V}$. If $V_{CC} = 16\text{ V}$, calculate R_1 and R_C to place Q point at $I_C = 2\text{ mA}$, $V_{CE} = 6\text{ volts}$.

