

Basic Electrical Engineering (TEE 101)

Lecture 26: Series AC circuits ($R - L$ and $R - C$) and Impedance

Content

This lecture covers:

Series R – L circuit

Series R – C circuit

Concept of Impedance (Z)

Series R – L AC circuit

This is the most general case met in practice as nearly all a.c. circuits contain both resistance and inductance. Fig. 1 shows a pure resistance of R ohms connected in series with a coil of pure inductance L henry.

Let V = r.m.s. value of the applied voltage

It is measured in I = r.m.s. value of the circuit current

$V_R = I R$ where V_R is in phase with I

$V_L = I X_L$ where V_L leads I by 90°

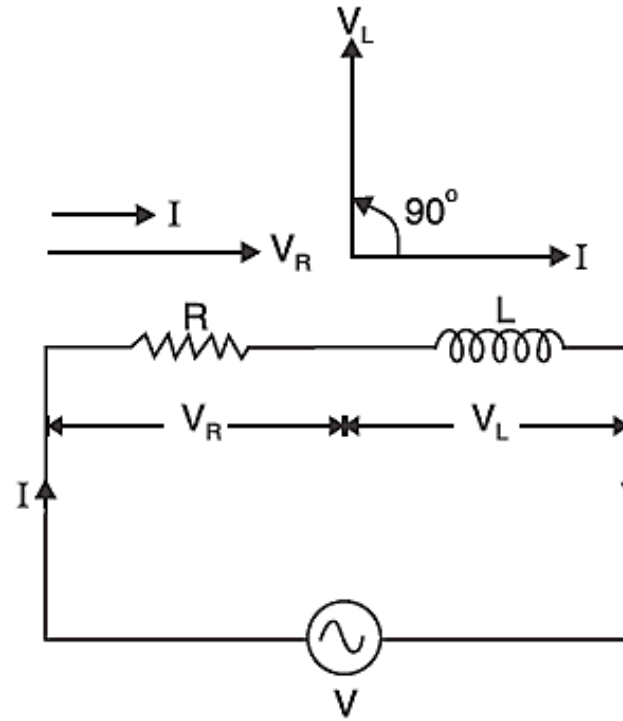


Fig. 1 circuit diagram

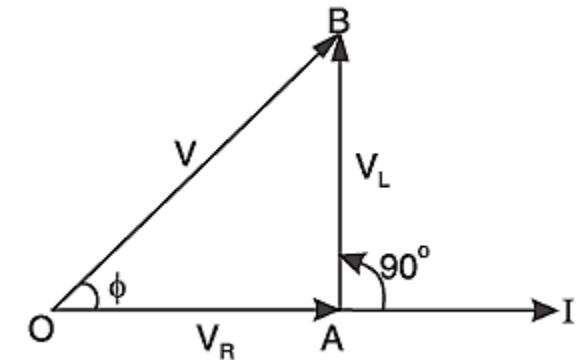


Fig. 2 Phasor Diagram

Taking current as the reference phasor, the phasor diagram of the circuit can be drawn as shown in Fig. 2.

The voltage drop $V_R (= I R)$ is in phase with current and is represented in magnitude and direction by the phasor OA .

The voltage drop $V_L (= I X_L)$ leads the current by 90° and is represented in magnitude and direction by the phasor AB . The applied voltage V is the phasor sum of these two drops *i.e.*

$$V = \sqrt{V_R^2 + V_L^2} = \sqrt{(IR)^2 + (IX_L)^2} = I \sqrt{R^2 + X_L^2}$$

$$I = \frac{V}{\sqrt{R^2 + X_L^2}}$$

The quantity $\sqrt{R^2 + X_L^2}$

offers opposition to current flow and is called **impedance** of the circuit. It is represented by Z and is measured in ohms (Ω).

$$I = \frac{V}{Z} \quad \text{where } Z = \sqrt{R^2 + X_L^2}$$

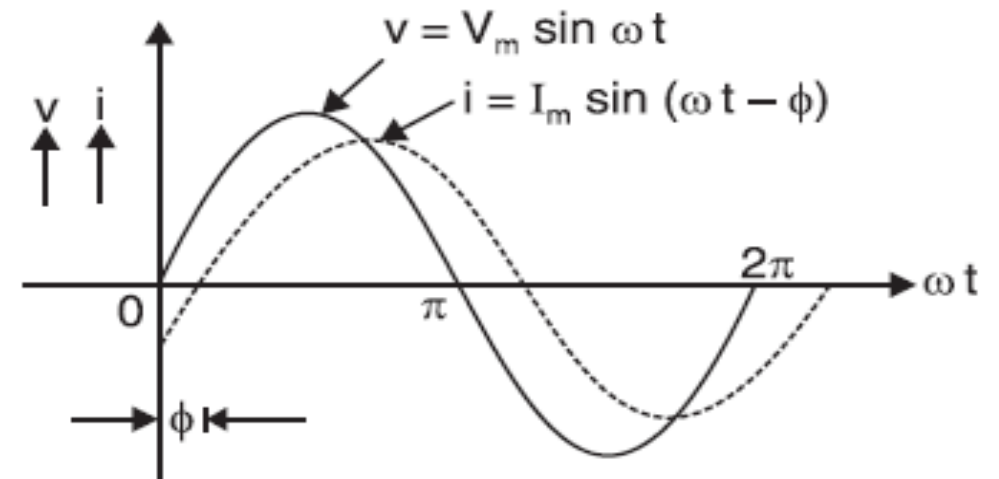


Fig. 3 Wave Diagram of series RL circuit

It is clear from the phasor diagram (fig. 2) and wave diagram (fig. 3) that circuit current I lags the applied voltage V by ϕ°

Series R – C AC circuit

Fig. 4 shows a resistance of R ohms connected in series with a capacitor of C farad.

Let V = r.m.s. value of the applied voltage

It is measured in I = r.m.s. value of the circuit current.

$V_R = I R$ where V_R is in phase with I

$V_C = I X_C$ where V_C lags I by 90°

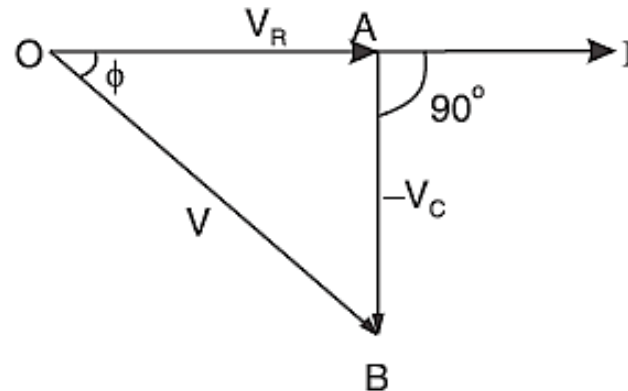


Fig. 5 Phasor Diagram

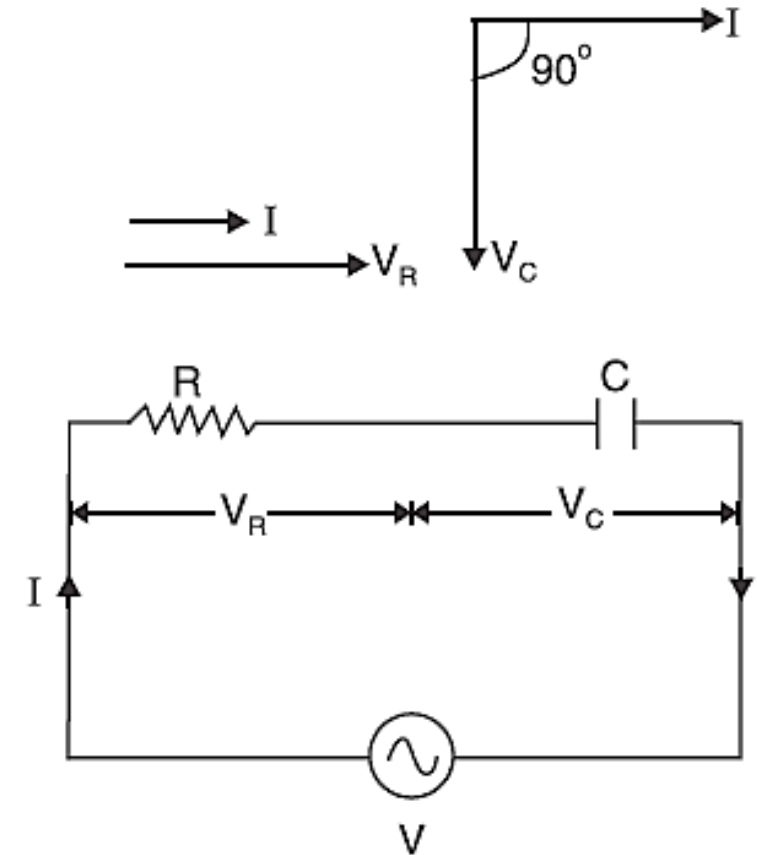


Fig. 4 circuit diagram

Taking current as the reference phasor, the phasor diagram of the circuit can be drawn as shown in Fig. 5

The voltage drop $V_R (= IR)$ is in phase with current and is represented in magnitude and direction by the phasor OA.

The voltage drop $V_C (= IX_C)$ lags behind the current by 90° and is represented in magnitude and direction by the phasor AB. The applied voltage V is the phasor sum of these two drops.

$$V = \sqrt{V_R^2 + (-V_C)^2} = \sqrt{(IR)^2 + (-IX_C)^2} = I \sqrt{R^2 + X_C^2}$$

$$I = \frac{V}{\sqrt{R^2 + X_C^2}}$$

The quantity $\sqrt{R^2 + X_C^2}$

offers opposition to current flow and is called **impedance** of the circuit. It is represented by Z and is measured in ohms (Ω).

$$I = \frac{V}{Z} \quad \text{where, } Z = \sqrt{R^2 + X_C^2}$$

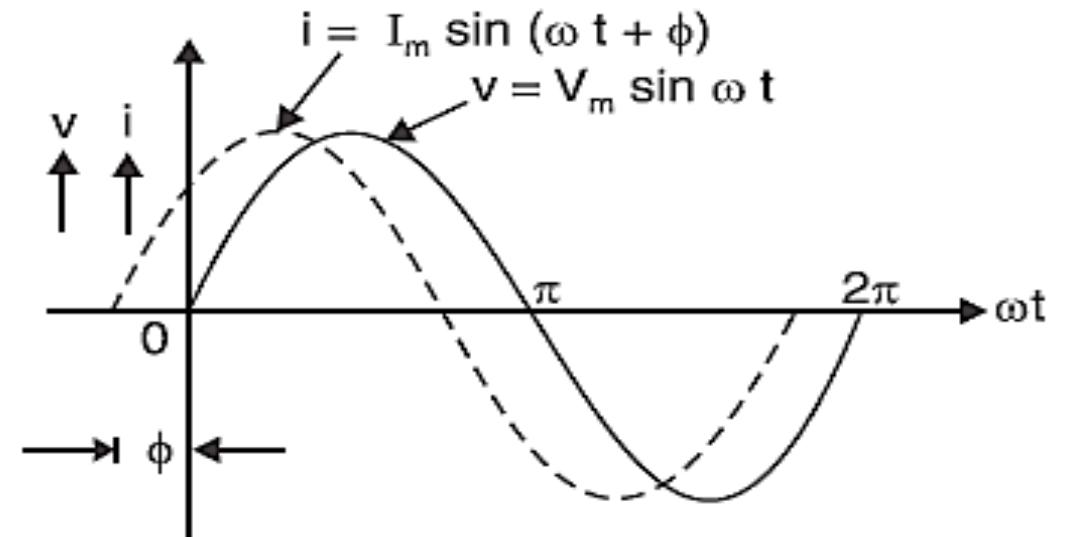


Fig. 6 Wave Diagram of series RC circuit

It is clear from the phasor diagram (fig. 5) and wave diagram (fig. 6) that circuit current I leads the applied voltage V by ϕ°

IMPEDANCE (Z)

Impedance. *The total opposition offered to the flow of alternating current by a circuit is called **impedance** Z of the circuit.*

Impedance consists of two components viz. resistance and reactance. Therefore, it can be expressed in these two components.

Let the impedance of an alternating current circuit is $Z=R+jX$ where, **R and X are known as resistance and reactance respectively**

It is clear from the above expression of Z is that, it is a complex number and hence can be geometrically represented in the same manner as a complex number. The geometrical representation is shown below.


The magnitude of impedance is given by, $|Z| = \sqrt{R^2 + X^2}$

For series R – L AC circuit: Impedance, $Z = \sqrt{R^2 + X_L^2}$ where $X_L = 2\pi fL$

The magnitude of impedance in R - L series circuit depends upon the values of R , L and the supply frequency f .

For series R – C AC circuit: Impedance, $Z = \sqrt{R^2 + X_C^2}$, where $X_C = \frac{1}{2\pi fC}$

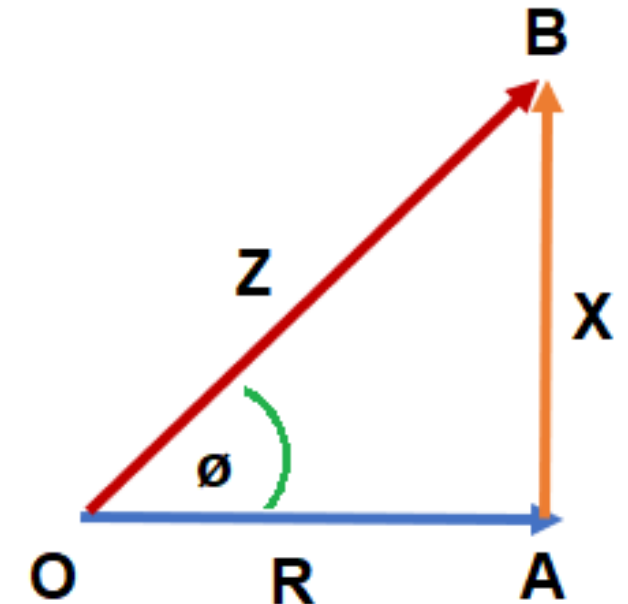The magnitude of impedance in R - C series circuit depends upon the values of R , C and the supply frequency f .



IMPEDANCE TRIANGLE

- The phasor diagram of a R - L series circuit is shown in Fig. 7.
- Dividing each side of the phasor diagram by the same factor I , we get a triangle whose sides represent R , X_L and Z .
- Such a triangle is known as *impedance triangle* (See Fig. 7 and 8).
- Just as in Fig. 7, the impedance triangle is also a right-angled triangle.
- Similarly, for R - C series circuit, the impedance triangle is shown in figure 8.

Impedance triangle is a useful concept in a.c. circuits as it enables us to calculate :

- (i) the impedance of the circuit *i.e.*,
- (ii) power factor of the circuit *i.e.*, $\cos \phi = R/Z$
- (iii) phase angle ϕ *i.e.*, $\tan \phi = X_L/R$
- (iv) whether current leads or lags the voltage.

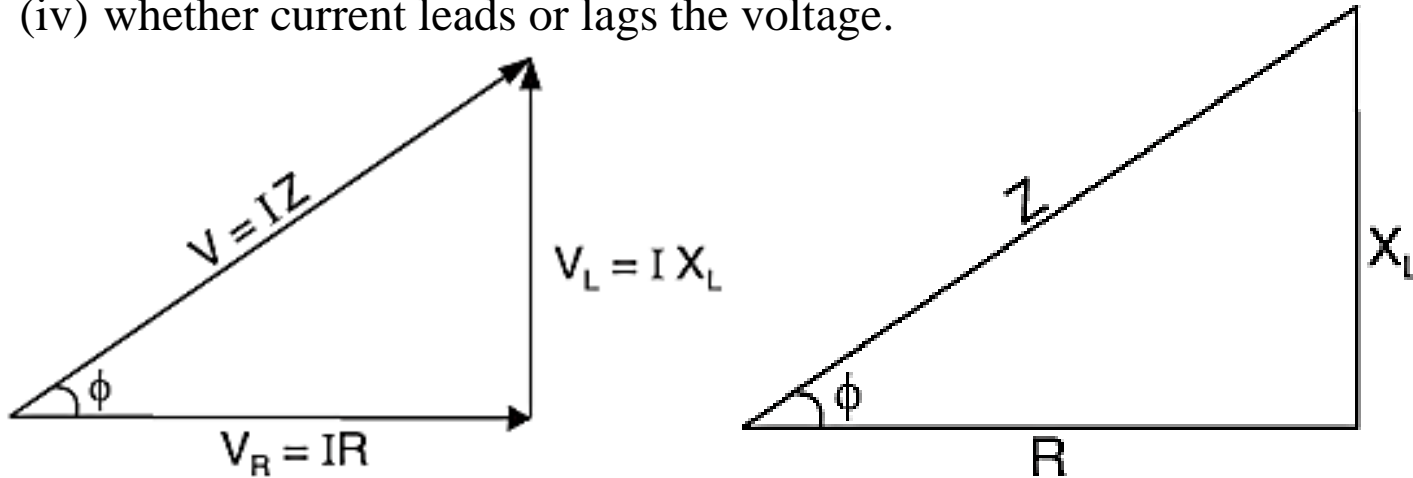


Fig. 7 Impedance Triangle of RL series circuit

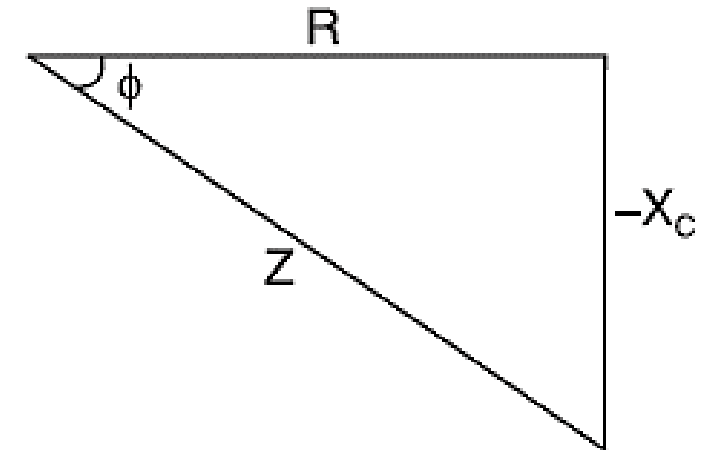


Fig. 8 Impedance Triangle of RC series circuit

Thank You