

Color	1 st band	2 nd band	3 rd band (Multiplier)	4 th band tolerance
B - Black	0	0	10^0	
Br - Brown	1	1	10^1	$\pm 1\%$
R - Red	2	2	10^2	$\pm 2\%$
O - Orange	3	3	10^3	
Y - Yellow	4	4	10^4	
G - Green	5	5	10^5	$\pm 0.5\%$
B - Blue	6	6	10^6	$\pm 0.25\%$
V - Violet	7	7	10^7	$\pm 0.1\%$
G - Grey	8	8	10^8	$\pm 0.05\%$
W - White	9	9	10^9	
Gold	—	—	0.1	$\pm 5\%$
Silver	—	—	0.01	$\pm 10\%$
None	—	—	—	$\pm 20\%$

Minimum

Four-Band Axial Resistors

5-Band Axial Resistors


Energy in a Resistor: Instantaneous Power absorbed in the resistor

$$p = V \times i = i^2 R \text{ (Watt)}$$

Therefore, the energy converted into heat energy is given by

$$W = \int_0^t p dt = \int_0^t i^2 R dt = i^2 R t \text{ Joules}$$

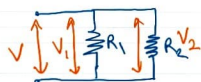Series & Parallel Arrangements of Resistors



$$R_{eq} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

Characteristics of Parallel Circuits


- 1- The Voltage across all the resistances is the same.
- 2- The total current is the sum of the currents flowing through the parallel resistances.

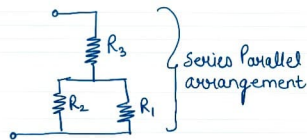1. The Voltage across all the resistances is the same.
2. The total current is the sum of the currents flowing through the parallel resistances.
3. The reciprocal of the equivalent resistance of a parallel circuit is equal to the sum of the reciprocal of the individual resistances.
4. The highest current passes through the highest conductance (with the lowest resistance).



The current through resistors in a series stays the same, but the voltage across each resistor can be different.

The sum of potential differences is equal to the total voltage.




$$R_{eq} = (R_1 \parallel R_2) + R_3$$

$$= \frac{R_1 \times R_2}{R_1 + R_2} + R_3$$

Characteristics of Series Circuits

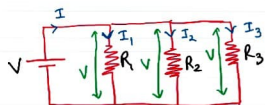1. The same current flows through each resistance.
2. The supply voltage, V , is the sum of the voltage drop across each resistance.
3. The equivalent resistance is equal to the sum of the individual resistances.



$$I = I_1 + I_2 + I_3$$

$$I_1 = \frac{V}{R_1}, \quad I_2 = \frac{V}{R_2}, \quad I_3 = \frac{V}{R_3}$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$


$$I = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$I = V \times \frac{1}{R_{eq}} ; R_{eq} = \frac{V}{I}$$

Minimum

Ques: Consider an electric circuit as shown below

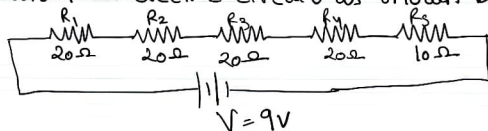Ques: Consider an electric circuit as shown below



(a) $R_{eq} = R_1 + R_2 + R_3 + R_4 + R_5$
 $= 20 + 20 + 20 + 20 + 10 = 90\Omega$

(b) Current through each resistor

$V = IR$
 $I = \frac{V}{R_{eq}} = \frac{9}{90} = 0.1 \text{ Amp}$

(c) Potential drop across each resistor.




$V = IR$

Potential drop across $R_1 = IR_1 = V_1$
 " " $R_2 = IR_2 = V_2$
 " " $R_3 = IR_3 = V_3$
 $IR_4 = V_4$
 $IR_5 = V_5$

$V = V_1 + V_2 + V_3 + V_4 + V_5$

Ques: Three resistances of values 20Ω , 100Ω & 50Ω are parallel to each other across a Voltage Source of 125 V .

Minimum

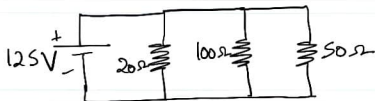


(a) $R_{eq} = ?$ $\frac{1}{R_{eq}} = \frac{1}{20} + \frac{1}{100} + \frac{1}{50}$

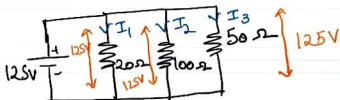(b) Current across each Resistor


$I_1 = \frac{V}{R} = \frac{125}{20} =$

$I_2 = \frac{125}{100}$, $I_3 = \frac{125}{50}$



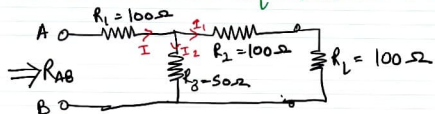
(c) Potential drop across each resistor will be same.

Ques: Calculate the equivalent Resistance of a given circ.





$$R_{AB} = R_{eq} = R_1 + (R_3 \parallel (R_2 + R_L))$$

$$= 140\Omega$$

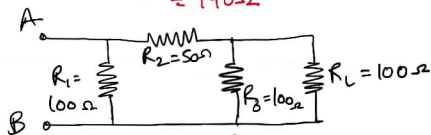
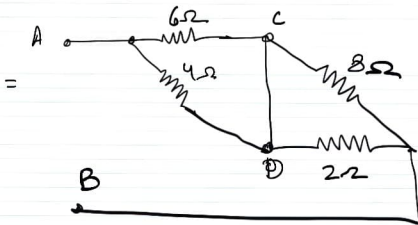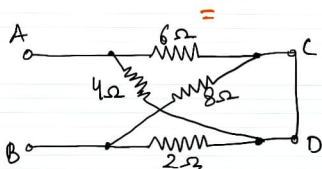
$$R_{AB} = [R_1 \parallel (R_2 + (R_3 \parallel R_L))]$$



$R_{AB} =$

