
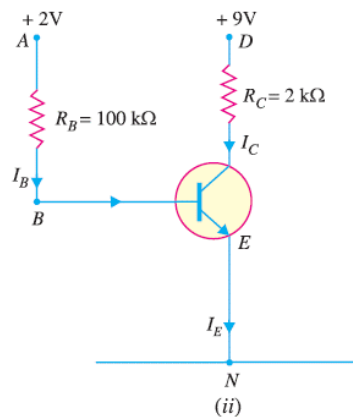


Assignment 4 | Dr Vivek Chamoli

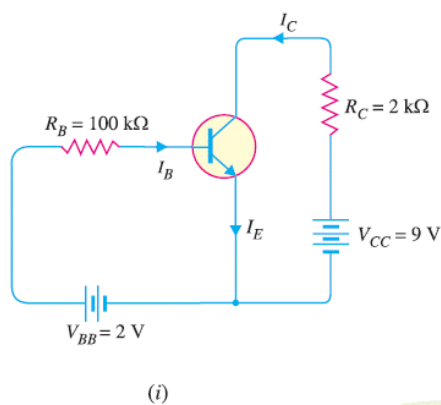
1. With the help of a neat diagram explain the operation of full wave bridge rectifier.
2. A half wave rectifier uses diode with forward resistance of $100\ \Omega$. If the input AC voltage is 220 V (rms) and the load resistance is of $2\text{ K}\Omega$. Determine (i) I_{\max} , I_{dc} and I_{rms} (ii) Load output voltage (iii) DC output power and AC input power (iv) ripple factor (v) TUF (vi) Rectification efficiency.
3. A regulator circuit uses zener diode of 30V , series resistance (R_S) is $3\text{K}\Omega$. if the input voltage is 60V , find the zener current (I_Z) when load resistance (R_L) is $20\text{K}\Omega$.
4. Explain the construction of BJT and input/output characteristics of CE configuration.
5. What is Q point? Derive equations for Self-Bias configuration of the transistor.
6. Following figure (i) shows biasing with base resistor method.
7. Determine the collector current I_C and collector-emitter voltage V_{CE} . Neglect small base-emitter voltage. Given that $\beta = 50$.

If R_B in this circuit is changed to $50\text{ k}\Omega$, find the new operating point.



8. Derive the mathematical relation between current gains α and β of a BJT. Also discuss the leakage currents I_{CBO} and I_{CEO} .

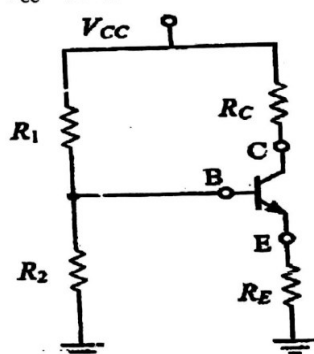
9. Consider the following voltage divider bias circuit of BJT. Determine the collector current I_C and collector to emitter voltage V_{CE} . Given, $R_1 = 60\text{ k}\Omega$, $R_2 = 7\text{ k}\Omega$, $R_C = 12\text{ k}\Omega$, $R_E = 1.7\text{ k}\Omega$, $V_{BE} = 0.7\text{ V}$, current gain $\beta = 50$ and $V_{CC} = 30\text{ V}$.



10.

- (b) Why is transistor biasing required ?
Determine the following for the BJT bias circuit shown in the figure given below.
Assume Si-BJT. Given that $\beta = 80$:

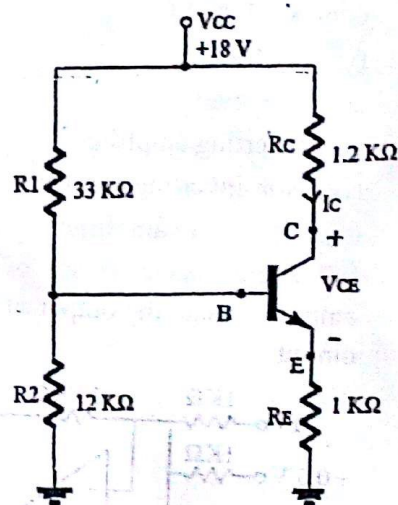- (i) Type of biasing
- (ii) I_C
- (iii) V_{CE}



11.

- (a) Write characteristics of an ideal Op-Amp.
Also discuss the concept of virtual ground.
- (b) Draw neat circuit diagrams and derive the output of the following Op-Amp based circuits :
 - (i) Adder
 - (ii) Subtractor
- (c) What do you mean by an inverting amplifier ? Discuss, how an Op-Amp can be used as a differentiator ?

12. Write down the characteristics for ideal op-amp. Explain voltage transfer curve for op-amp.


13. Design an Adder circuit using an op-amp to get the output expression as

$$i. V_{out} = -(V_1 + 10 V_2 + 100 V_3)$$

where V_1 , V_2 and V_3 are the inputs. Given that $R_f = 100k\Omega$

14. Draw the diagrams and derive the equations for op-amp as differentiator and integrator.

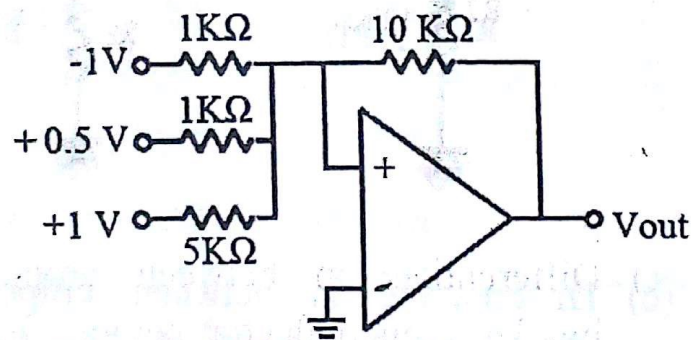15. (a) Describe the concept of virtual ground in op-amp. circuits. Draw the circuit diagram of an integrator using op-amp. and explain its working.
- (b) Write short notes on the following in context of op-amps. :
- (i) CMRR
 - (ii) Slew rate
 - (iii) Inverting amplifier
 - (iv) Non-inverting amplifier
 - (v) Unity gain amplifier
- (c) Enlist the characteristics of an ideal op-amp. Calculate the output of the following circuit :



- 16.
- (a) In a center tap full wave rectifier, the load resistance is $1\text{ k}\Omega$. Each diode has forward resistance of $10\ \Omega$. The voltage across the secondary winding is 220 V . Find the values of the following :
 - (i) Peak value of current
 - (ii) Average value of current
 - (iii) RMS value of current
 - (iv) Rectification efficiency
 - (v) Ripple factor
 - (b) Derive the following parameters for the half wave rectifier :
 - (i) Average current
 - (ii) RMS Voltage
 - (iii) Rectification efficiency
 - (c) Write short notes on the following :
 - (i) Zener diode
 - (ii) LED
- 17.
- (b) Explain input and output characteristics of CB configuration of npn transistor. Also derive the relation $I_C = \beta I_B + (1 + \beta) I_{CBO}$.
 - (c) A CE amplifier employing an NPN transistor has load resistance R_C connected between collector and V_{CC} supply of $+16\text{V}$. For biasing a resistor R_1 is connected between collector and base. Resistor $R_2 = 1\text{ k}\Omega$ is connected between base and ground and Resistor $R_E = 1\text{ k}\Omega$ is connected between emitter and ground. Draw the circuit diagram and calculate the value of R_1 and R_C if $V_{CE} = 6\text{ V}$, $V_{BE} = 0.2\text{ V}$ and $\alpha = 0.985$.

18.

- (b) Fig. 1 shows a simple Zener diode voltage regulator circuit. The voltage across the load is to be maintained constant 12 V while the load current varies from 0 to 200 mA. Find the value of V_Z and R_S . Also find the maximum power rating of Zener diode :

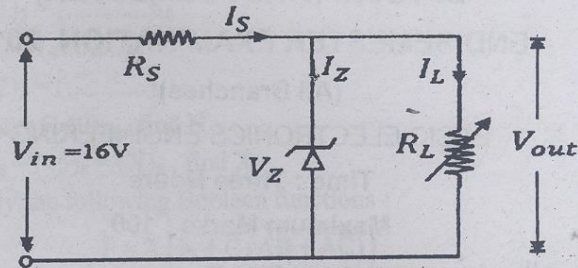


Fig. 1

19.

- (a) Explain common base configuration of BJT with suitable diagram. Also draw its input and output characteristics.
- (b) A silicon BJT with $\beta = 100$, is shown in Fig. 2, compute the transistor parameters i_B , i_C , i_E and V_{CE} . In which mode the BJT is operating ?
- (c) Explain all three configurations of a BJT in terms of :
- Input impedance
 - Output impedance
 - Voltage gain
 - Current gain

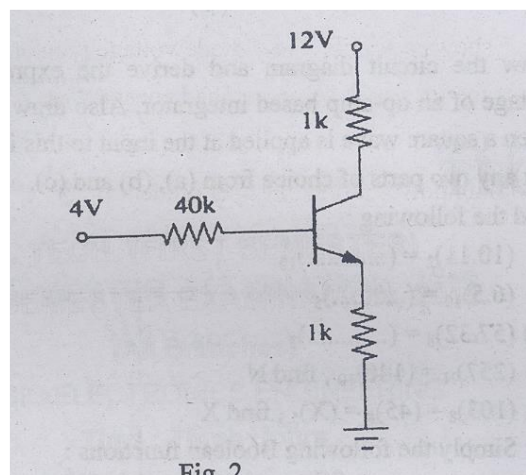


Fig. 2

20.

- (a) Explain the ideal characteristics of an op-amp in terms of input impedance, output impedance, differential and common mode voltage gain, common mode rejection ratio, slew rate. Under what condition the open loop gain become infinite ?
- (b) An op-amp based differential amplifier is shown in Fig. 3. Derive the expression for its output voltage (V_{out}) in terms of V_1 and V_2 . Also find the value of the output voltage, assume $V_1 = 2$ V, $V_2 = 3$ V, when $R_1 = R_2 = 1$ k Ω , $R_3 = 5$ k Ω , and $R_4 = 8$ k Ω .

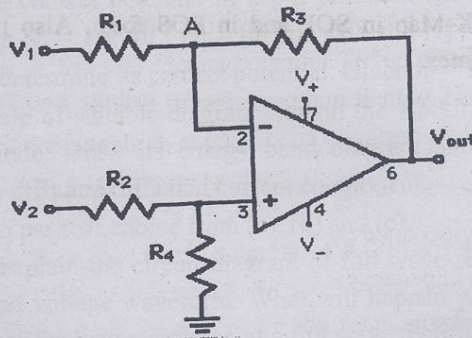


Fig. 3

21.

- (c) A full-wave rectifier uses a double diode with each element having a constant forward resistance of 500Ω . The transformer r. m. s. secondary voltage from the centre tap to each plate is 300 V, the load resistance of 2.5 k Ω . Determine :
- d. c. out power (P_{dc}) and a. c. input power (P_{ac}).
 - Efficiency (η).